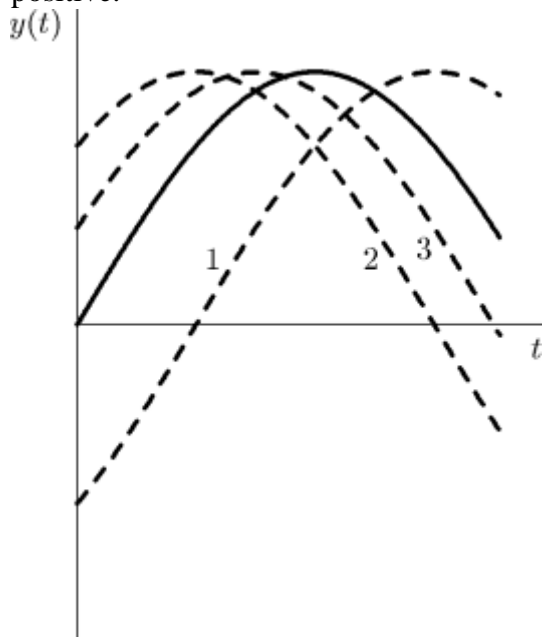


Name: _____ Date: _____

- ___ 1. A series RL circuit is connected to an emf source of angular frequency ω . The current:
- A) leads the applied emf by $\tan^{-1}(\omega L/R)$ D) leads the applied emf by $\tan^{-1}(\omega R/L)$
 B) lags the applied emf by $\tan^{-1}(\omega L/R)$ E) is zero
 C) lags the applied emf by $\tan^{-1}(\omega R/L)$
- ___ 2. A current of 10 A in a certain inductor results in a stored energy of 40 J. When the current is changed to 5 A in the opposite direction, the stored energy changes by:
 A) 20 J B) 30 J C) 40 J D) 50 J E) 60 J
- ___ 3. In a purely inductive circuit, the current lags the voltage by:
 A) zero D) three-fourths of a cycle
 B) one-fourth of a cycle E) one cycle
 C) one-half of a cycle
- ___ 4. An LC circuit has a capacitance of $30 \mu\text{F}$ and an inductance of 15 mH. At time $t = 0$ the charge on the capacitor is $10 \mu\text{C}$ and the current is 20 mA. The maximum charge on the capacitor is:
 A) $8.9 \mu\text{C}$ B) $10 \mu\text{C}$ C) $12 \mu\text{C}$ D) $17 \mu\text{C}$ E) $24 \mu\text{C}$
- ___ 5. A resistor, an inductor, and a capacitor are connected in parallel to a sinusoidal source of emf. Which of the following is true?
 A) The currents in all branches are in phase.
 B) The potential differences across all branches are in phase.
 C) The current in the capacitor branch leads the current in the inductor branch by one-fourth of a cycle
 D) The potential difference across the capacitor branch leads the potential difference across the inductor branch by one-fourth of a cycle.
 E) The current in the capacitor branch lags the current in the inductor branch by one-fourth of a cycle.

- ___ **11.** A charged capacitor and an inductor are connected in series. At time $t = 0$ the current is zero, but the capacitor is charged. If T is the period of the resulting oscillations, the next time after $t = 0$ that the energy stored in the electric field of the capacitor is a maximum is:
A) T B) $T/4$ C) $T/2$ D) T E) $2T$
- ___ **12.** An RLC series circuit has $L = 100$ mH and $C = 1$ μ F. It is connected to a 1000-Hz source and the source emf is found to lead the current by 75° . The value of R is:
A) 12.6Ω B) 126Ω C) 175Ω D) 1750Ω E) 1810Ω
- ___ **13.** An inductance L and a resistance R are connected in series to an ideal battery. A switch in the circuit is closed at time 0, at which time the current is zero. The energy stored in the inductor is a maximum:
A) just after the switch is closed
B) at the time $t = L/R$ after the switch is closed
C) at the time $t = L/R$ after the switch is closed
D) at the time $t = 2L/R$ after the switch is closed
E) a long time after the switch is closed
- ___ **14.** An RLC circuit has an inductance of 25 mH and a capacitance of 5.0 μ F. The charge on the capacitor does NOT oscillate but rather decays exponentially to zero. The resistance in the circuit must be:
A) greater than or equal to $20,000\Omega$
B) less than $20,000\Omega$ but greater than $10,000\Omega$
C) less than $10,000\Omega$ but greater than $5,000\Omega$
D) less than $5,000\Omega$ but greater than 0
E) 0

- ___ 15. In the diagram, the function $y(t) = y_m \sin(\omega t)$ is plotted as a solid curve. The other three curves have the form $y(t) = y_m \sin(\omega t + \phi)$, where ϕ is between $-\pi/2$ and $+\pi/2$. Rank the curves according to the value of ϕ , from the most negative to the most positive.



- A) 1, 2, 3 B) 2, 3, 1 C) 3, 2, 1 D) 1, 3, 2 E) 2, 1, 3
- ___ 16. An ac generator producing 10 V (rms) at 200 rad/s is connected in series with a 50- Ω resistor, a 400-mH inductor, and a 200- μ F capacitor. The rms voltage (in volts) across the inductor is:
 A) 2.5 B) 3.4 C) 6.7 D) 10.0 E) 10.8
- ___ 17. The rapid exponential decay in just a few cycles of the charge on the plates of capacitor in an *RLC* circuit might be due to:
 A) a large inductance D) a large resistance
 B) a large capacitance E) a small resistance
 C) a small capacitance

Answer Key

1. B
Origin: Chapter 33- Electromagnetic Oscillations and Alternating Current, 49
2. B
Origin: Chapter 33- Electromagnetic Oscillations and Alternating Current, 5
3. B
Origin: Chapter 33- Electromagnetic Oscillations and Alternating Current, 48
4. D
Origin: Chapter 33- Electromagnetic Oscillations and Alternating Current, 34
5. B
Origin: Chapter 33- Electromagnetic Oscillations and Alternating Current, 71
6. A
Origin: Chapter 33- Electromagnetic Oscillations and Alternating Current, 37
7. D
Origin: Chapter 33- Electromagnetic Oscillations and Alternating Current, 33
8. C
Origin: Chapter 33- Electromagnetic Oscillations and Alternating Current, 18
9. E
Origin: Chapter 33- Electromagnetic Oscillations and Alternating Current, 61
10. B
Origin: Chapter 33- Electromagnetic Oscillations and Alternating Current, 12
11. C
Origin: Chapter 33- Electromagnetic Oscillations and Alternating Current, 13
12. B
Origin: Chapter 33- Electromagnetic Oscillations and Alternating Current, 65
13. E
Origin: Chapter 33- Electromagnetic Oscillations and Alternating Current, 2
14. A
Origin: Chapter 33- Electromagnetic Oscillations and Alternating Current, 39
15. D
Origin: Chapter 33- Electromagnetic Oscillations and Alternating Current, 64
16. E
Origin: Chapter 33- Electromagnetic Oscillations and Alternating Current, 78
17. D
Origin: Chapter 33- Electromagnetic Oscillations and Alternating Current, 41
18. D
Origin: Chapter 33- Electromagnetic Oscillations and Alternating Current, 73
19. C
Origin: Chapter 33- Electromagnetic Oscillations and Alternating Current, 38
20. A
Origin: Chapter 33- Electromagnetic Oscillations and Alternating Current, 68